

1. Write a Verilog code for 2X4 decoder.

DATA FLOW MODELLING:

```
module decoder(d0,d1,d2,d3,e,a,b);  
    input e,a,b;  
    output d0,d1,d2,d3;  
    assign d0=e&~a&~b;  
    assign d1=e&~a&b;  
    assign d2=e&a&~b;  
    assign d3=e&a&b;  
endmodule
```

//testbench//

```
module testbench();  
  
    reg t_e, t_a, t_b;  
    wire t_d0, t_d1, t_d2, t_d3;  
  
    decoder dut(.e(t_e), .a(t_a), .b(t_b), .d0(t_d0), .d1(t_d1),  
    .d2(t_d2), .d3(t_d3));  
  
    initial begin  
        t_e = 0; t_a = 1; t_b = 1;  
        #100;  
        t_e = 1; t_a = 0; t_b = 0;  
        #100;  
        t_e = 1; t_a = 0; t_b = 1;  
        #100;  
        t_e = 1; t_a = 1; t_b = 0;  
        #100;  
    end  
endmodule
```

```
t_e = 1; t_a = 1; t_b = 1;
$finish();
end
endmodule
```

BEHAVIORAL MODELLING:

```
module decoder(d0,d1,d2,d3,e,a,b);
input e,a,b;
output d0,d1,d2,d3;
reg d0,d1,d2,d3;
always @(e,a,b)
begin
d0 = e & ~ a & ~ b;
d1 = e & ~ a & b;
d2 = e & a & ~ b;
d3 = e & a & b;
end
endmodule
```

```
//testbench//
//verilog code
module decoder(d0,d1,d2,d3,e,a,b);
input e, a, b;
output d0, d1, d2, d3;
assign d0 = e & ~a & ~b;
assign d1 = e & ~a & b;
assign d2 = e & a & ~b;
assign d3 = e & a & b;
endmodule
```

```

                                //testbench//
module testbench();
    reg t_e, t_a, t_b;
    wire t_d0, t_d1, t_d2, t_d3;

    decoder dut(.e(t_e), .a(t_a), .b(t_b), .d0(t_d0), .d1(t_d1),
.d2(t_d2), .d3(t_d3));

    initial begin
        t_e = 0; t_a = 1; t_b = 1;
        #100;
        t_e = 1; t_a = 0; t_b = 0;
        #100;
        t_e = 1; t_a = 0; t_b = 1;
        #100;
        t_e = 1; t_a = 1; t_b = 0;
        #100;
        t_e = 1; t_a = 1; t_b = 1;
        $finish();
    end
endmodule

```

GATE LEVEL MODELLING:

```

module decoder(d0,d1,d2,d3,a,b);
    input a,b;
    output d0,d1,d2,d3;
    wire w1,w2;
    not g1(w1,a);
    not g2(w2,b);
    and g3(d0,w1,w2);

```

```
and g4(d1,w1,b);
and g5(d2,a,w2);
and g6(d3,a,b);
endmodule
```

```
//testbench//
module testbench();
  reg a, b;
  wire d0, d1, d2, d3;

  decoder dut(.a(a), .b(b), .d0(d0), .d1(d1), .d2(d2), .d3(d3));

  initial begin
    $dumpfile("testbench.vcd");
    $dumpvars(0, testbench);

    // Test case 1
    a = 0; b = 0;
    #10;

    // Test case 2
    a = 0; b = 1;
    #10;

    // Test case 3
    a = 1; b = 0;
    #10;


    // Test case 4
    a = 1; b = 1;
```

```
#10;
```

```
$finish;
```

```
end
```

```
endmodule
```

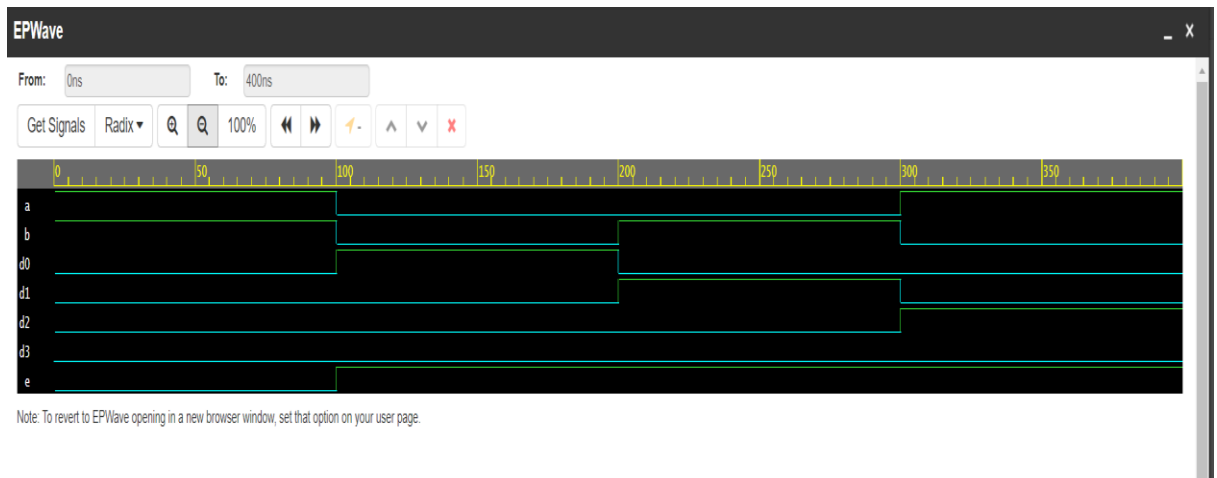

2. Write a Verilog code for Full subtractor.

Dataflow modelling:

```
module full_subtractor(
    bout, d, a, b, c
);
    input a, b, c;
    output bout, d;

    assign d = a ^ b ^ c;
    assign bout = (~a & b) || (c & ~(a ^ b));
endmodule

//Testbench//

module testbench();
    reg t_a, t_b, t_c;
    wire t_bout, t_d;
    full_subtractor dut(.a(t_a), .b(t_b), .c(t_c), .bout(t_bout),
    .d(t_d));
    initial begin
        $dumpfile("testbench.vcd");
        $dumpvars(0, testbench);
    end

    initial begin
        t_a = 0; t_b = 0; t_c = 0; // Test case 1
        #10;
        t_a = 0; t_b = 0; t_c = 1; // Test case 2
```

```

#10;
t_a = 0; t_b = 1; t_c = 0; // Test case 3
#10;
t_a = 0; t_b = 1; t_c = 1; // Test case 4
#10;
t_a = 1; t_b = 0; t_c = 0; // Test case 5
#10;
t_a = 1; t_b = 0; t_c = 1; // Test case 6
#10;
t_a = 1; t_b = 1; t_c = 0; // Test case 7
#10;
t_a = 1; t_b = 1; t_c = 1; // Test case 8
#10;
$finish();
end
endmodule

```

Behavioral modelling:

```

module full_subtractor(bout,d,a,b,c);
  input a,b,c;
  output bout,d;
  wire w1,w2,w3,w4,w5;
  xor g3(w1,a,b);
  not g1(w2,a);
  not g2(w3,w1);
  and g4(w4,w2,b);
  and g5(w5,w3,c);
  xor g6(d,w1,c);
  or g7(bout,w4,w5);
endmodule

```

```
                                //Testbench//  
module testbench;  
    reg a, b, c;  
    wire bout, d;  
  
    full_subtractor dut(  
        .a(a),  
        .b(b),  
        .c(c),  
        .bout(bout),  
        .d(d)  
    );  
  
    initial begin  
        $dumpfile("testbench.vcd");  
        $dumpvars(0, testbench);  
  
        // Test case 1  
        a = 0; b = 0; c = 0;  
        #10;  
  
        // Test case 2  
        a = 0; b = 0; c = 1;  
        #10;  
  
        // Test case 3  
        a = 0; b = 1; c = 0;  
        #10;  
  
        // Test case 4
```



```
a = 0; b = 1; c = 1;  
#10;
```


```
// Test case 5  
a = 1; b = 0; c = 0;  
#10;
```

```
// Test case 6  
a = 1; b = 0; c = 1;  
#10;
```

```
// Test case 7  
a = 1; b = 1; c = 0;  
#10;
```

```
// Test case 8  
a = 1; b = 1; c = 1;  
#10;
```

```
$finish;  
end  
endmodule
```

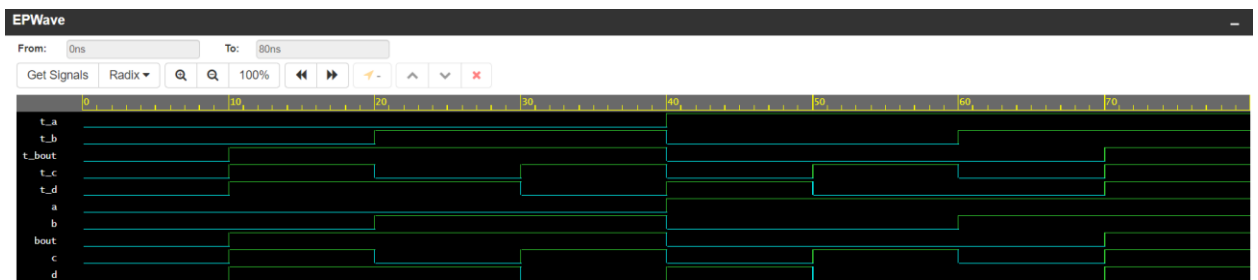

3. Write a Verilog code for 2-bit comparator.

DATAFLOW MODELLING:

```
module comparator_2bit(  
    input [1:0] A,  
    input [1:0] B,  
    output reg EQ,  
    output reg GT,  
    output reg LT  
);  
  
    assign EQ = (A[1] & ~B[1] & A[0] & ~B[0]) | (~A[1] & B[1] & ~A[0] &  
B[0]);  
    assign GT = (A[1] & ~B[1]) | ((A[1] ^ B[1]) & ~A[0]);  
    assign LT = (B[1] & ~A[1]) | ((A[1] ^ B[1]) & ~B[0]);  
  
endmodule
```

```
//Testbench//
```

```
module testbench;
```

```
    reg [1:0] A;
```

```
    reg [1:0] B;
```

```
    wire EQ, GT, LT;
```

```
    // Instantiate the comparator
```

```
    comparator_2bit uut (
```

```
        .A(A),
```

```
        .B(B),
```

```
        .EQ(EQ),
```

```
        .GT(GT),
```

```
        .LT(LT)
```

```
    );
```

```
    initial begin
```

```
        $dumpfile("testbench.vcd");
```

```
        $dumpvars(0, testbench);
```

```
    end
```

```
    // Initialize inputs and monitor outputs
```

```
    initial begin
```

```
$monitor("Time = %0t: A = %b, B = %b, EQ = %b, GT = %b, LT = %b", $time, A, B, EQ, GT, LT);
```

```
A = 2'b00;
```

```
B = 2'b01;
```

```
#5;
```

```
A = 2'b10;
```

```
B = 2'b01;
```

```
#5;
```

```
A = 2'b01;
```

```
B = 2'b01;
```

```
#5;
```

```
// Add more test cases here
```

```
$finish;
```

```
end
```

```
endmodule
```

Behavioral modelling:

```
module comparator_2bit(
```

```
    input [1:0] A,
```

```
    input [1:0] B,
```

```
    output reg EQ,
```

```
    output reg GT,
```

```
    output reg LT
```

```
);
```

```
    always @* begin
```

```
        EQ = (A == B);
```

```
        GT = (A > B);
```

```
        LT = (A < B);
```

```
    end
```

```
endmodule
```

```
//Testbench//
```

```
module testbench;
```

```
    reg [1:0] A;
```

```
    reg [1:0] B;
```

```
    wire EQ, GT, LT;
```

```
    // Instantiate the comparator
```

```

comparator_2bit uut (
    .A(A),
    .B(B),
    .EQ(EQ),
    .GT(GT),
    .LT(LT)
);
initial begin
    $dumpfile("testbench.vcd");
    $dumpvars(0,testbench);
end

// Initialize inputs and monitor outputs
initial begin
    $monitor("Time = %0t: A = %b, B = %b, EQ = %b, GT = %b, LT = %b", $time, A, B, EQ, GT, LT);

    A = 2'b00;
    B = 2'b01;
    #5;

    A = 2'b10;
    B = 2'b01;
    #5;

    A = 2'b01;
    B = 2'b01;
    #5;

    // Add more test cases here


```

```

    $finish;
end

endmodule

```

 

4. Write a Verilog code for 3 bit binary to gray convertor.

Dataflow modelling:

```

module binary_to_gray(g,b);
    input [2:0]b;

```

```
output [2:0]g;  
assign g[2]=b[2];  
assign g[1]=b[2]^b[1];  
assign g[0]=b[1]^b[0];  
endmodule
```

```
//Testbench//
```

```
module testbench();  
  reg [2:0]t_b;  
  wire [2:0]t_g;  
  binary_to_gray dut(.g(t_g), .b(t_b));  
  initial begin  
    $dumpfile("testbench.vcd");  
    $dumpvars(0,testbench);  
  end  
  initial begin  
    t_b[2]=0;t_b[1]=0;t_b[0]=0;  
    #100  
    t_b[2]=0;t_b[1]=0;t_b[0]=1;  
    #100  
    t_b[2]=0;t_b[1]=1;t_b[0]=0;  
    #100  
    t_b[2]=0;t_b[1]=1;t_b[0]=1;  
    #100  
    t_b[2]=1;t_b[1]=0;t_b[0]=0;  
    #100  
    t_b[2]=1;t_b[1]=0;t_b[0]=1;  
    #100  
    t_b[2]=1;t_b[1]=1;t_b[0]=0;
```



```

#100
t_b[2]=1;t_b[1]=1;t_b[0]=1;
#100
$finish();
end
endmodule


```

Behavioral modelling:

```

module binary_to_gray(g,b);
    input [2:0]b;
    output [2:0]g;
    reg [2:0]g;
    always @(b[2],b[1],b[0]);
    initial begin
        g[2]=b[2];
        g[1]=b[2]^b[1];
        g[0]=b[1]^b[0];
    end
endmodule

```

 

5. Write a Verilog code for BCD to excess 3 convertors.

Dataflow modelling:

```
module bcd_to_excess3(e,b);
    input [3:0]b;
    output [3:0]e;
    assign e[3]=((b[3]) || (b[2]&b[0] || (b[2]&b[1])));
    assign e[2]=((b[2]&~b[1]&~b[0]) || (~b[2]&b[0]) || (~b[2]&b[1]));
    assign e[1]=(~b[1]&~b[0] || (b[1]&b[0]));
    assign e[0]=~b[0];
endmodule

//Testbench//

module testbench;

    reg [3:0] b;
    wire [3:0] e;

    // Instantiate the bcd_to_excess3 module
    bcd_to_excess3 uut (
        .b(b),
```

```
        .e(e)
    );
initial begin
    $dumpfile("testbench.vcd");
    $dumpvars(0,testbench);
end
```

```
// Initialize inputs and monitor outputs
```

```
initial begin
    $monitor("Time = %0t: BCD = %b, Excess-3 = %b", $time, b, e);
```

```
    b = 4'b0000;
```

```
    #5;
```

```
    b = 4'b0101;
```

```
    #5;
```

```
    b = 4'b1001;
```

```
    #5;
```

```
    b = 4'b1111;
```

```
    #5;
```

```
// Add more test cases here
```

```
$finish;
```

```
end
```

```
endmodule
```

Behavioral modelling:

```
module bcd_to_excess3(
```

```
    input [3:0] b,
```

```
    output reg [3:0] e
```

```
);
```

```
    always @* begin
```

```
        e[3] = (b[3]) || (b[2] & b[0]) || (b[2] & b[1]);
```

```
        e[2] = (b[2] & ~b[1] & ~b[0]) || (~b[2] & b[0]) || (~b[2] & b[1]);
```

```
        e[1] = (~b[1] & ~b[0]) || (b[1] & b[0]);
```

```
        e[0] = ~b[0];
```

```
    end
```

```
endmodule
```

From: 0ns

To: 20ns

Get Signals

Radix ▾

🔍

🔍

100%

⏮


⏭

🔍

⬆

⬇

✖

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

ASSIGNMENT 2

[1] Design 4-bit Ripple Carry Adder with the help of 1-bit adder.

```
module full_adder(  
    input a,  
    input b,  
    input cin,  
    output sum,  
    output carry  
);  
    assign sum = a ^ b ^ cin;  
    assign carry = (a & b) | (cin & (a ^ b));  
endmodule
```

```
module rca_4bit(  
    output [3:0] s,  
    output cout,  
    input [3:0] a,  
    input [3:0] b,  
    input cin  
);
```

```

wire c0, c1, c2, c3;
full_adder fa0(s[0], c0, a[0], b[0], cin);
full_adder fa1(s[1], c1, a[1], b[1], c0);
full_adder fa2(s[2], c2, a[2], b[2], c1);
full_adder fa3(s[3], c3, a[3], b[3], c2);
assign cout = c3;
endmodule

                                //Testbench//

module testbench;
    reg [3:0] a;
    reg [3:0] b;
    reg cin;
    wire [3:0] s;
    wire cout;

    rca_4bit rca_inst(
        .s(s),
        .cout(cout),
        .a(a),
        .b(b),
        .cin(cin)
    );

```

```
initial begin
    $dumpfile("testbench.vcd");
    $dumpvars(0,testbench);
end
```


```
initial begin
    $display("a  b  cin | s  cout");
    $monitor("%b %b %b | %b %b", a, b, cin, s, cout);

    a = 4'b0010;
    b = 4'b1101;
    cin = 0;
    #10;

    a = 4'b1111;
    b = 4'b0001;
    cin = 1;
    #10;

    $finish;
end
```


endmodule

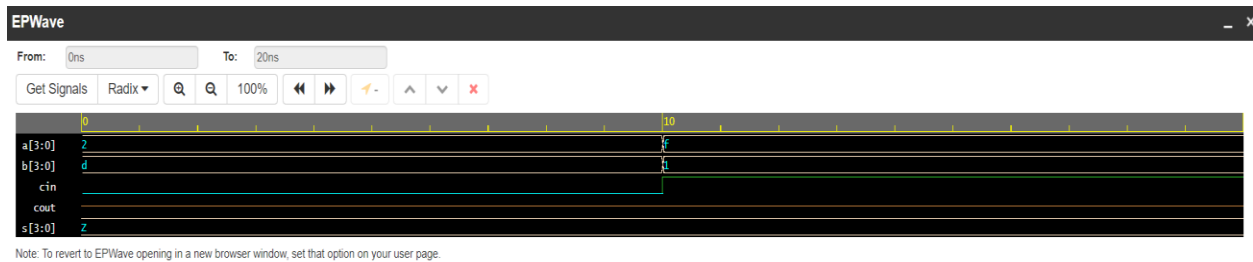

2] Design D-flipflop and reuse it to implement 4- bit Johnson Counter.

Dataflow modelling:

```
module Johnson_Counter (  
    input wire clk,  
    input wire reset,  
    output reg [3:0] counter_output  
);  
  
    reg [3:0] q_temp;  
  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            q_temp <= 4'b0001; // Initial value  
        else  
            q_temp <= {q_temp[2:0], q_temp[3]};  
    end  
endmodule
```

```
end
```

```
assign counter_output = q_temp;
```

```
endmodule
```

```
//Testbench//
```

```
module testbench;
```

```
reg clk;
```

```
reg reset;
```

```
wire [3:0] counter_output;
```

```
Johnson_Counter dut (
```

```
    .clk(clk),
```

```
    .reset(reset),
```

```
    .counter_output(counter_output)
```

```
);
```

```
initial begin
```

```
    $dumpfile("testbench.vcd");
```

```
    $dumpvars(0,testbench);
```

```
end
```

always begin

```
#5 clk = ~clk; // Toggle the clock every 5 time units
```

end

initial begin

```
clk = 0;
```

```
reset = 1; // Start with reset active
```

```
#10 reset = 0; // Deactivate reset after 10 time units
```


```
// Wait for a few clock cycles to observe the counter sequence
```

#50;

```
$finish; // End simulation
```

end

endmodule

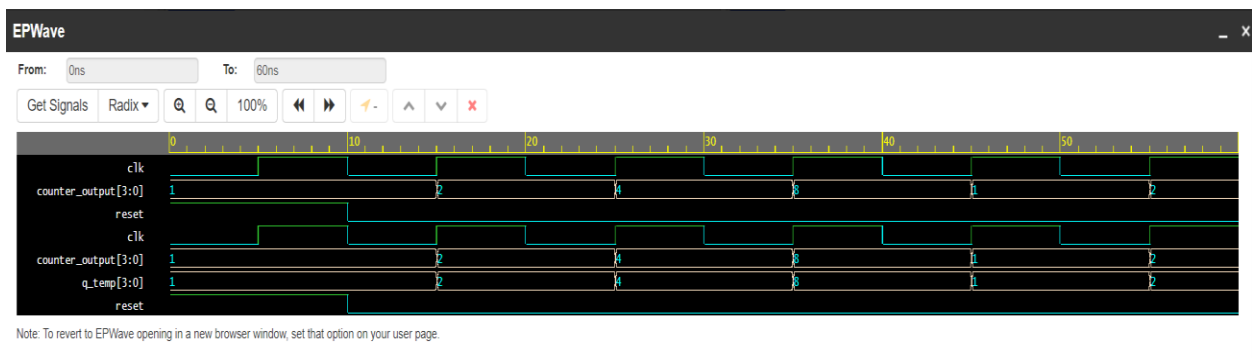

[3] Reuse 2:1 Mux code to implement 8:1 Mux.

```
module Mux2to1 (  
    input wire sel,  
    input wire d0,  
    input wire d1,  
    output wire y  
);  
  
    assign y = (sel == 1'b0) ? d0 : d1;
```

endmodule

```
module Mux8to1 (  
    input wire [2:0] sel,  
    input wire [7:0] d,  
    output wire y  
);  
  
    wire [1:0] sel0, sel1;  
    wire [3:0] d0, d1;  
    wire [1:0] d2;
```

```
// First stage of 2:1 muxes
```

```
Mux2to1 mux0 (
```

```
    .sel(sel[0]),
```

```
    .d0(d[0]),
```

```
    .d1(d[1]),
```

```
    .y(d0[0])
```

```
);
```

```
Mux2to1 mux1 (
```

```
    .sel(sel[0]),
```

```
    .d0(d[2]),
```

```
    .d1(d[3]),
```

```
    .y(d0[1])
```

```
);
```

```
Mux2to1 mux2 (
```

```
    .sel(sel[0]),
```

```
    .d0(d[4]),
```

```
    .d1(d[5]),
```

```
    .y(d0[2])
```

```
);
```

```
Mux2to1 mux3 (
```

```
    .sel(sel[0]),
```

```
    .d0(d[6]),
```

```
    .d1(d[7]),
```

```
    .y(d0[3])
```

```
);
```

```
// Second stage of 2:1 muxes
```

```
Mux2to1 mux4 (
```

```
    .sel(sel[1]),
```

```
    .d0(d0[0]),
```

```
    .d1(d0[1]),
```

```
    .y(d1[0])
```

```
);
```

```
Mux2to1 mux5 (
```

```
    .sel(sel[1]),
```

```
    .d0(d0[2]),
```

```
    .d1(d0[3]),
```

```
    .y(d1[1])
```

```
);
```

```
Mux2to1 mux6 (  
    .sel(sel[1]),  
    .d0(d0[0]),  
    .d1(d0[1]),  
    .y(d1[2])  
);
```

```
Mux2to1 mux7 (  
    .sel(sel[1]),  
    .d0(d0[2]),  
    .d1(d0[3]),  
    .y(d1[3])  
);
```

// Third stage of 2:1 muxes

```
Mux2to1 mux8 (  
    .sel(sel[2]),  
    .d0(d1[0]),  
    .d1(d1[1]),  
    .y(y)  
);
```

```
endmodule
```

```
//Testbench//
```

```
module testbench();
```

```
    reg [2:0] sel;
```

```
    reg [7:0] d;
```

```
    wire y;
```

```
    Mux8to1 dut (
```

```
        .sel(sel),
```

```
        .d(d),
```

```
        .y(y)
```

```
    );
```

```
    initial begin
```

```
        $dumpfile("testbench.vcd");
```

```
        $dumpvars(0,testbench);
```

```
    end
```

```
    initial begin
```

```
        // Initialize inputs
```

```
        sel = 3'b000; // Select input 0 (000 in binary)
```



```
d = 8'b10101010; // Arbitrary data input
```

```
// Wait for a few time units before changing inputs
```

```
#10;
```

```
// Test with different selection values
```

```
sel = 3'b001; // Select input 1 (001 in binary)
```

```
#10;
```

```
sel = 3'b010; // Select input 2 (010 in binary)
```

```
#10;
```


```
sel = 3'b111; // Select input 7 (111 in binary)
```

```
#10;
```

```
$finish; // End simulation
```

```
end
```

```
endmodule
```

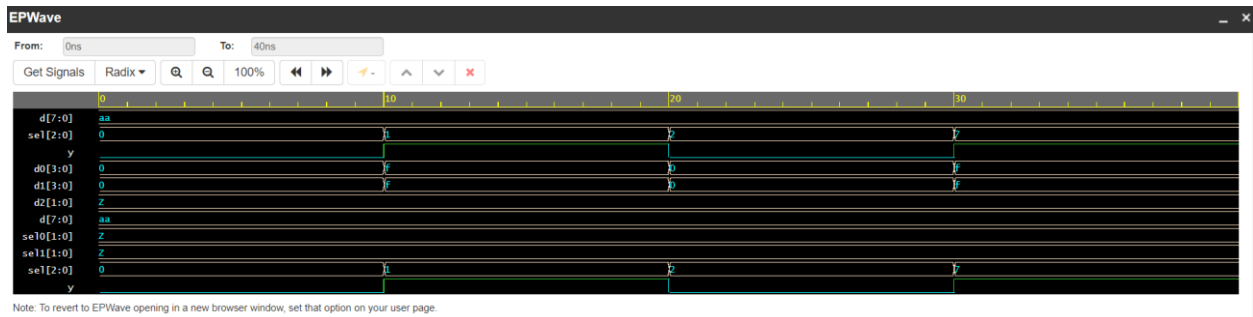

[4] Design a Full Subtractor with Gate Level Modeling Style.(use primitive gates)

```
module full_subtractor_gate_level(
```

```
    input x,
```

```
    input y,
```

```
    input z,
```

```
    output difference,
```

```
    output borrow
```

```
);
```

```
    xor_21 x1(x,y,k1);
```

```
    xor_21 x2(k1,z,difference);
```

```
    and_21 a1(~x,y,k2);
```

```
    and_21 a2(~x,z,k3);
```

```
    and_21 a3(y,z,k4);
```

```
or_21 o1(k2,k3,k5);  
or_21 o2(k5,k4,borrow);
```

```
endmodule
```

```
//Testbench//
```

```
module xor_21 (  
    input wire a,  
    input wire b,  
    output wire y  
);
```

```
    assign y = a ^ b;
```

```
endmodule
```

```
module and_21 (  
    input wire a,  
    input wire b,  
    output wire y  
);
```

```
    assign y = a & b;
```

```
endmodule
```

```
module or_21 (  
    input wire a,  
    input wire b,  
    output wire y  
);  
    assign y = a | b;  
endmodule
```

```
module testbench;  
    reg x, y, z;  
    wire difference, borrow;  
  
    full_subtractor_gate_level uut(  
        .x(x),  
        .y(y),  
        .z(z),  
        .difference(difference),  
        .borrow(borrow)  
    );  
  
    initial begin  
        $dumpfile("testbench.vcd");
```

```
$dumpvars(0, testbench);
```

```
// Initialize inputs
```

```
x = 0; y = 0; z = 0;
```

```
// Wait for a few time units before changing inputs
```

```
#10;
```

```
// Change inputs and observe outputs
```

```
x = 1; y = 0; z = 0;
```

```
#10;
```

```
x = 1; y = 1; z = 0;
```

```
#10;
```

```
x = 1; y = 0; z = 1;
```

```
#10;
```

```
x = 1; y = 1; z = 1;
```

```
#10;
```

```
// End simulation
```


```

    $finish;

end

endmodule

```

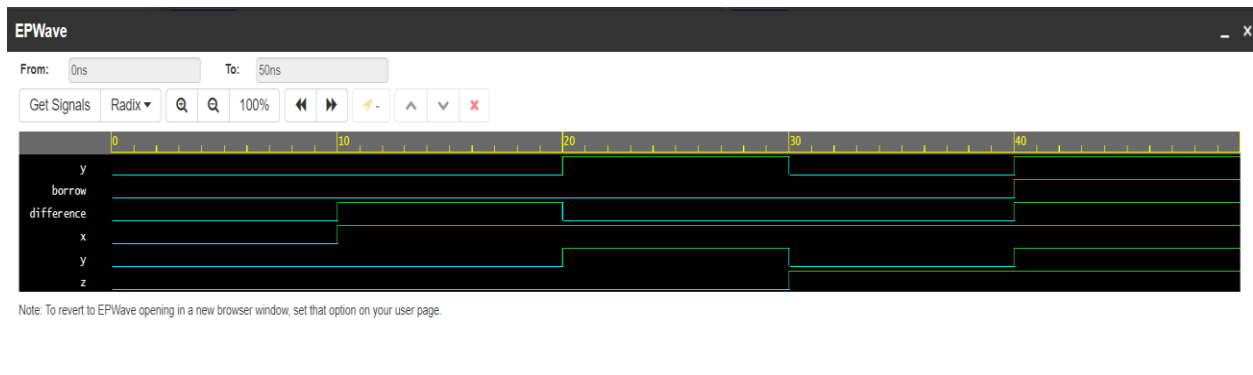

[5] Design a 2X4 decoder using gate level modelling.

```

module decoder_24_gate_level(

```

```

    input x1,
    input x2,
    output y1,
    output y2,
    output y3,
    output y4
);

```

```

    and a1(y1,~x1,~x2);
    and a2(y2,~x1,x2);
    and a3(y3,x1,~x2);

```

```
and a4(y4,x1,x2);
```

```
endmodule
```

```
//Testbench//
```

```
module decoder_24_tb;
```

```
reg x1,x2;
```

```
wire y1,y2,y3,y4;
```

```
initial begin
```

```
    $monitor(" %t | x1 = %b | x2 = %b | y1 = %b | y2 = %b | y3 = %b | y4  
= %b ",$time,x1,x2,y1,y2,y3,y4);
```

```
end
```

```
decoder_24_gate_level uut(x1,x2,y1,y2,y3,y4);
```

```
initial begin
```

```
#000 x1=0; x2=0;
```

```
#100 x1=0; x2=1;
```

```
#100 x1=1; x2=0;
```

```
#100 x1=1; x2=1;
```

```
#100 $finish;
```

```
end
```

```
initial begin
```

```
    $dumpfile("dump.vcd");
```

```
    $dumpvars(0);
```

```
end
```

```
endmodule
```

[6] Design a 4x1 mux using operators. (use data flow)

```
module Mux4x1 (
```

```
    input wire [3:0] data,
```

```
    input wire [1:0] sel,
```

```
    output wire out
```

```
);
```

```
    assign out = (sel == 2'b00) ? data[0] :
```

```
        (sel == 2'b01) ? data[1] :
```



```
(sel == 2'b10) ? data[2] :  
(sel == 2'b11) ? data[3] : 1'bx;
```

```
Endmodule
```

```
//Testbench//
```

```
module testbench_mux4x1;
```

```
    reg [3:0] data;
```

```
    reg [1:0] sel;
```

```
    wire out;
```

```
    Mux4x1 uut (
```

```
        .data(data),
```

```
        .sel(sel),
```

```
        .out(out)
```

```
    );
```


```
    initial begin
```

```
        $dumpfile("testbench_mux4x1.vcd");
```

```
        $dumpvars(0, testbench_mux4x1);
```

```
        // Initialize inputs
```
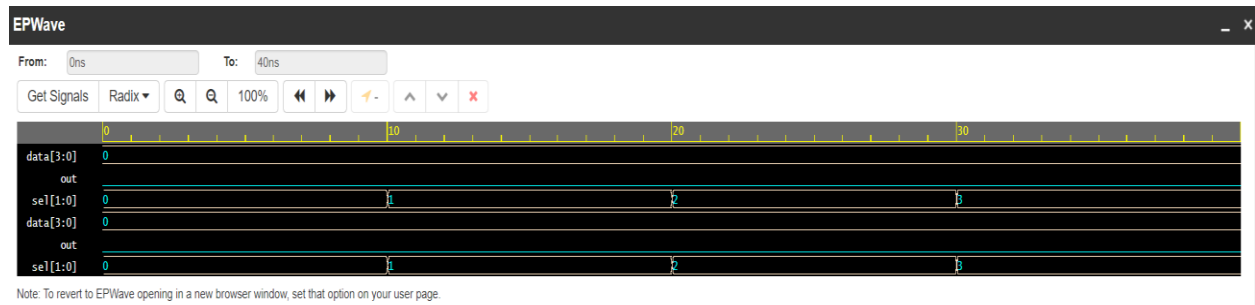
```
data = 4'b0000;  
sel = 2'b00;  
  
// Wait for a few time units before changing inputs  
#10;  
  
// Test with different selection values  
sel = 2'b01;  
#10;  
  
sel = 2'b10;  
#10;  
  
sel = 2'b11;  
#10;  
  
// End simulation  
$finish;  
end  
endmodule
```



[7] Design a Full adder using half adder.

```

module Half_Adder (
    input wire A,
    input wire B,
    output wire Sum,
    output wire Carry
);

    assign Sum = A ^ B;
    assign Carry = A & B;

endmodule

module Full_Adder (
    input wire A,
    input wire B,
    input wire Cin,

```

```
    output wire Sum,  
    output wire Cout  
);
```

```
    wire HA_Sum1, HA_Carry1, HA_Carry2;
```

```
    Half_Adder HA1 (.A(A), .B(B), .Sum(HA_Sum1), .Carry(HA_Carry1));  
    Half_Adder HA2 (.A(HA_Sum1), .B(Cin), .Sum(Sum),  
    .Carry(HA_Carry2));
```

```
    assign Cout = HA_Carry1 | HA_Carry2;
```

```
endmodule
```

```
    //Testbench//
```

```
module testbench;
```

```
    reg A, B, Cin;
```

```
    wire Sum, Cout;
```

```
    Full_Adder uut (
```

```
        .A(A),
```

```
        .B(B),
```

```
.Cin(Cin),  
.Sum(Sum),  
.Cout(Cout)  
);
```

```
initial begin
```

```
    $dumpfile("testbench.vcd");  
    $dumpvars(0, testbench);
```

```
// Test cases
```

```
A = 0; B = 0; Cin = 0;  
#10;
```

```
A = 0; B = 0; Cin = 1;  
#10;
```

```
A = 0; B = 1; Cin = 0;  
#10;
```

```
A = 0; B = 1; Cin = 1;  
#10;
```

A = 1; B = 0; Cin = 0;

#10;

A = 1; B = 0; Cin = 1;

#10;

A = 1; B = 1; Cin = 0;

#10;

A = 1; B = 1; Cin = 1;

#10;

\$finish;

end

endmodule

